1. Which of the following function is lossless and why? find the Cover I and foster-I expansion for the correspon-ZLs) - 52+ 105+24 s²+ 8s + 15 7 (s) - 55 + 1053 + 245 54+652+5 What are the properties of LC driving point impedance function? Which of the following function is valid LC driving point impedance function? State with $\frac{Z(1)}{S^{4}+6s^{2}+5}$, $\frac{Z(1)}{S^{4}+6s^{2}+5}$, $\frac{Z(1)}{S^{2}+16}$, $\frac{Z(1)}{S^{2}+16}$ tind the Courer second form of valid driving point impedance function (3+3+3) Which of the following is valid lossless function? State with reason · Pick one of the valid LC lossless functions and synthesize it using foster If
and Courer If methods: (3+3+3)

Z(s) ~ (32+4) 111) Z(s) = S6+ 4,4+ 852 (3+31 What are the properties of RC impedance function? Synthesize the given RC impedance in foster & Cauer form.

Z(s) ~ 3(s+2)(s+4) 3(3+3)